

*26.1 (a) $Q = C(\Delta V) = (4.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 4.80 \times 10^{-5} \text{ C} = \boxed{48.0 \mu\text{C}}$

(b) $Q = C(\Delta V) = (4.00 \times 10^{-6} \text{ F})(1.50 \text{ V}) = 6.00 \times 10^{-6} \text{ C} = \boxed{6.00 \mu\text{C}}$

26.4 (a) $C = 4\pi\epsilon_0 R$

$R = \frac{C}{4\pi\epsilon_0} = k_e C = (8.99 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2)(1.00 \times 10^{-12} \text{ F}) = \boxed{8.99 \text{ mm}}$

(b) $C = 4\pi\epsilon_0 R = \frac{4\pi(8.85 \times 10^{-12} \text{ C}^2)(2.00 \times 10^{-3} \text{ m})}{\text{N} \cdot \text{m}^2} = \boxed{0.222 \text{ pF}}$

(c) $Q = CV = (2.22 \times 10^{-13} \text{ F})(100 \text{ V}) = \boxed{2.22 \times 10^{-11} \text{ C}}$

26.11 (a) $C = \frac{l}{2k_e \ln\left(\frac{b}{a}\right)} = \frac{50.0}{2(8.99 \times 10^9) \ln\left(\frac{7.27}{2.58}\right)} = \boxed{2.68 \text{ nF}}$

(b) Method 1: $\Delta V = 2k_e \lambda \ln\left(\frac{b}{a}\right)$

$\lambda = q/l = \frac{8.10 \times 10^{-6} \text{ C}}{50.0 \text{ m}} = 1.62 \times 10^{-7} \text{ C/m}$

$\Delta V = 2(8.99 \times 10^9)(1.62 \times 10^{-7}) \ln\left(\frac{7.27}{2.58}\right) = \boxed{3.02 \text{ kV}}$

Method 2: $\Delta V = \frac{Q}{C} = \frac{8.10 \times 10^{-6}}{2.68 \times 10^{-9}} = \boxed{3.02 \text{ kV}}$

26.21 (a) $\frac{1}{C_s} = \frac{1}{15.0} + \frac{1}{3.00} \quad C_s = 2.50 \mu\text{F}$

$C_p = 2.50 + 6.00 = 8.50 \mu\text{F}$

$C_{eq} = \left(\frac{1}{8.50 \mu\text{F}} + \frac{1}{20.0 \mu\text{F}}\right)^{-1} = \boxed{5.96 \mu\text{F}}$




(b) $Q = (\Delta V)C = (15.0 \text{ V})(5.96 \mu\text{F}) = \boxed{89.5 \mu\text{C}}$ on $20.0 \mu\text{F}$

$\Delta V = \frac{Q}{C} = \frac{89.5 \mu\text{C}}{20.0 \mu\text{F}} = 4.47 \text{ V}$

$15.0 - 4.47 = 10.53 \text{ V}$

$Q = (\Delta V)C = (10.53)(6.00 \mu\text{F}) = \boxed{63.2 \mu\text{C}}$ on $6.00 \mu\text{F}$

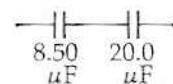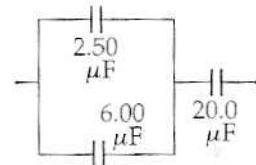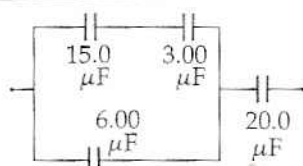$89.5 - 63.2 = \boxed{26.3 \mu\text{C}}$ on $15.0 \mu\text{F}$ and $3.00 \mu\text{F}$



*26.32

$U = \frac{1}{2} C(\Delta V)^2$

The circuit diagram is shown at the right.



(a) $C_p = C_1 + C_2 = 25.0 \mu\text{F} + 5.00 \mu\text{F} = 30.0 \mu\text{F}$

$U = \frac{1}{2} (30.0 \times 10^{-6})(100)^2 = \boxed{0.150 \text{ J}}$

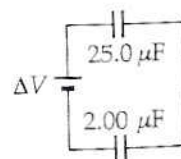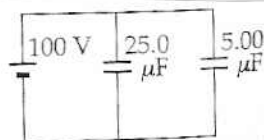(b) $C_s = \left(\frac{1}{C_1} + \frac{1}{C_2}\right)^{-1} = \left(\frac{1}{25.0 \mu\text{F}} + \frac{1}{5.00 \mu\text{F}}\right)^{-1} = 4.17 \mu\text{F}$

$U = \frac{1}{2} C(\Delta V)^2$

$\Delta V = \sqrt{\frac{2U}{C}} = \sqrt{\frac{(0.150)(2)}{4.17 \times 10^{-6}}} = \boxed{268 \text{ V}}$



26.43 $C = \frac{\kappa \epsilon_0 A}{d}$ or $95.0 \times 10^{-9} = \frac{3.70(8.85 \times 10^{-12})(0.0700)l}{(0.0250 \times 10^{-3})}$

$l = \boxed{1.04 \text{ m}}$