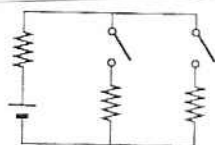


28.4 (a) Here $\mathcal{E} = I(R+r)$, so $I = \frac{\mathcal{E}}{R+r} = \frac{12.6 \text{ V}}{(5.00 \Omega + 0.0800 \Omega)} = 2.48 \text{ A}$

Then, $\Delta V = IR = (2.48 \text{ A})(5.00 \Omega) = \boxed{12.4 \text{ V}}$



(b) Let I_1 and I_2 be the currents flowing through the battery and the headlights, respectively.

Then, $I_1 = I_2 + 35.0 \text{ A}$, and $\mathcal{E} - I_1 r - I_2 R = 0$

so $\mathcal{E} = (I_2 + 35.0 \text{ A})(0.0800 \Omega) + I_2(5.00 \Omega) = 12.6 \text{ V}$

giving $I_2 = 1.93 \text{ A}$

Thus, $\Delta V_2 = (1.93 \text{ A})(5.00 \Omega) = \boxed{9.65 \text{ V}}$

28.15

$R_p = \left(\frac{1}{3.00} + \frac{1}{1.00} \right)^{-1} = 0.750 \Omega$

$R_s = (2.00 + 0.750 + 4.00) \Omega = 6.75 \Omega$

$I_{\text{battery}} = \frac{\Delta V}{R_s} = \frac{18.0 \text{ V}}{6.75 \Omega} = 2.67 \text{ A}$

$\mathcal{P} = I^2 R$: $\mathcal{P}_2 = (2.67 \text{ A})^2 (2.00 \Omega)$

$\mathcal{P}_2 = \boxed{14.2 \text{ W}}$ in 2.00Ω




$\mathcal{P}_4 = (2.67 \text{ A})^2 (4.00 \Omega) = \boxed{28.4 \text{ W}}$ in 4.00Ω

$\Delta V_2 = (2.67 \text{ A})(2.00 \Omega) = 5.33 \text{ V}$, $\Delta V_4 = (2.67 \text{ A})(4.00 \Omega) = 10.67 \text{ V}$

$\Delta V_p = 18.0 \text{ V} - \Delta V_2 - \Delta V_4 = 2.00 \text{ V}$ ($= \Delta V_3 = \Delta V_1$)

$\mathcal{P}_3 = \frac{(\Delta V_3)^2}{R_3} = \frac{(2.00 \text{ V})^2}{3.00 \Omega} = \boxed{1.33 \text{ W}}$ in 3.00Ω

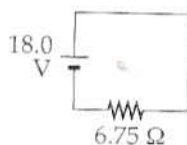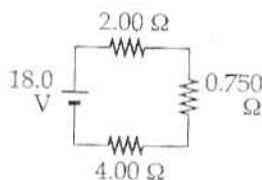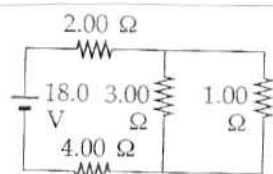$\mathcal{P}_1 = \frac{(\Delta V_1)^2}{R_1} = \frac{(2.00 \text{ V})^2}{1.00 \Omega} = \boxed{4.00 \text{ W}}$ in 1.00Ω



28.25 Using Kirchhoff's rules,

$12.0 - (0.0100)I_1 - (0.0600)I_3 = 0$

$10.0 + (1.00)I_2 - (0.0600)I_3 = 0$


and $I_1 = I_2 + I_3$

$12.0 - (0.0100)I_2 - (0.0700)I_3 = 0$

$10.0 + (1.00)I_2 - (0.0600)I_3 = 0$

Solving simultaneously, $I_2 = \boxed{0.283 \text{ A downward}}$ in the dead battery,

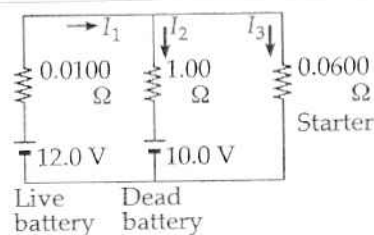and $I_3 = \boxed{171 \text{ A downward}}$ in the starter.



28.30 (a) $I(t) = -I_0 e^{-t/RC}$

$$I_0 = \frac{Q}{RC} = \frac{5.10 \times 10^{-6} \text{ C}}{(1300 \Omega)(2.00 \times 10^{-9} \text{ F})} = 1.96 \text{ A}$$

$$I(t) = -(1.96 \text{ A}) \exp\left[\frac{-9.00 \times 10^{-6} \text{ s}}{(1300 \Omega)(2.00 \times 10^{-9} \text{ F})}\right] = \boxed{-61.6 \text{ mA}}$$

(b) $q(t) = Q e^{-t/RC} = (5.10 \mu\text{C}) \exp\left[\frac{-8.00 \times 10^{-6} \text{ s}}{(1300 \Omega)(2.00 \times 10^{-9} \text{ F})}\right] = \boxed{0.235 \mu\text{C}}$

(c) The magnitude of the current is $\boxed{I_0 = 1.96 \text{ A}}$

28.48 (a) $\mathcal{P} = I^2 R = I^2 \left(\frac{\rho l}{A}\right) = \frac{(1.00 \text{ A})^2 (1.70 \times 10^{-8} \Omega \cdot \text{m})(16.0 \text{ ft})(0.3048 \text{ m / ft})}{\pi(0.512 \times 10^{-3} \text{ m})^2} = \boxed{0.101 \text{ W}}$

(b) $\mathcal{P} = I^2 R = 100(0.101 \Omega) = \boxed{10.1 \text{ W}}$