

32.4

$$L = \mu_0 n^2 A \ell \quad \text{so} \quad n = \sqrt{\frac{L}{\mu_0 A \ell}} = \boxed{7.80 \times 10^3 \text{ turns/m}}$$

32.7

$$\mathcal{E}_{\text{back}} = -\mathcal{E} = L \frac{dI}{dt} = L \frac{d}{dt} (I_{\text{max}} \sin \omega t) = L \omega I_{\text{max}} \cos \omega t = (10.0 \times 10^{-3})(120\pi)(5.00) \cos \omega t$$


$$\mathcal{E}_{\text{back}} = (6.00\pi) \cos(120\pi t) = \boxed{(18.8 \text{ V}) \cos(377t)}$$

$$*32.19 \quad (a) \quad \tau = L/R = 2.00 \times 10^{-3} \text{ s} = \boxed{2.00 \text{ ms}}$$

$$(b) \quad I = I_{\text{max}} (1 - e^{-t/\tau}) = \left(\frac{6.00 \text{ V}}{4.00 \Omega} \right) (1 - e^{-0.250/2.00}) = \boxed{0.176 \text{ A}}$$

$$(c) \quad I_{\text{max}} = \frac{\mathcal{E}}{R} = \frac{6.00 \text{ V}}{4.00 \Omega} = \boxed{1.50 \text{ A}}$$

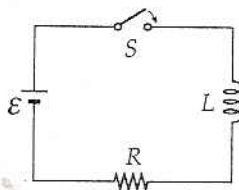
$$(d) \quad 0.800 = 1 - e^{-t/2.00 \text{ ms}} \rightarrow t = -(2.00 \text{ ms}) \ln(0.200) = \boxed{3.22 \text{ ms}}$$



$$*32.36 \quad (a) \quad U = \frac{1}{2} LI^2 = \frac{1}{2} (4.00 \text{ H})(0.500 \text{ A})^2 = \boxed{0.500 \text{ J}}$$

$$(b) \quad \frac{dU}{dt} = LI = (4.00 \text{ H})(1.00 \text{ A}) = 4.00 \text{ J/s} = \boxed{4.00 \text{ W}}$$
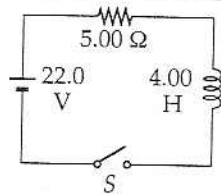
$$(c) \quad \mathcal{P} = (\Delta V)I = (22.0 \text{ V})(0.500 \text{ A}) = \boxed{11.0 \text{ W}}$$



32.50

When the switch has been closed for a long time, battery, resistor, and coil carry constant current $I_{\text{max}} = \mathcal{E}/R$. When the switch is opened, current in battery and resistor drops to zero, but the coil carries this same current for a moment as oscillations begin in the LC loop.

We interpret the problem to mean that the voltage amplitude of these oscillations is ΔV , in $\frac{1}{2}C(\Delta V)^2 = \frac{1}{2}LI_{\text{max}}^2$.

$$\text{Then,} \quad L = \frac{C(\Delta V)^2}{I_{\text{max}}^2} = \frac{C(\Delta V)^2 R^2}{\mathcal{E}^2} = \frac{(0.500 \times 10^{-6} \text{ F})(150 \text{ V})^2 (250 \Omega)^2}{(50.0 \text{ V})^2} = \boxed{0.281 \text{ H}}$$

