

33.7

$$\Delta V_{\max} = 15.0 \text{ V} \quad \text{and} \quad R_{\text{total}} = 8.20 \, \Omega + 10.4 \, \Omega = 18.6 \, \Omega$$

$$I_{\max} = \frac{\Delta V_{\max}}{R_{\text{total}}} = \frac{15.0 \text{ V}}{18.6 \, \Omega} = 0.806 \text{ A} = \sqrt{2} I_{\text{rms}}$$

$$\mathcal{P}_{\text{speaker}} = I_{\text{rms}}^2 R_{\text{speaker}} = \left(\frac{0.806 \text{ A}}{\sqrt{2}} \right)^2 (10.4 \, \Omega) = \boxed{3.38 \text{ W}}$$

33.12

$$\omega = 2\pi f = 2\pi(60.0 / \text{s}) = 377 \text{ rad / s}$$

$$X_L = \omega L = (377 / \text{s})(0.0200 \text{ V} \cdot \text{s} / \text{A}) = 7.54 \, \Omega$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{X_L} = \frac{120 \text{ V}}{7.54 \, \Omega} = 15.9 \text{ A}$$

$$I_{\max} = \sqrt{2} I_{\text{rms}} = \sqrt{2} (15.9 \text{ A}) = 22.5 \text{ A}$$

$$i(t) = I_{\max} \sin \omega t = (22.5 \text{ A}) \sin \left(\frac{2\pi(60.0)}{\text{s}} \cdot \frac{1 \text{ s}}{180} \right) = (22.5 \text{ A}) \sin 120^\circ = 19.5 \text{ A}$$

$$U = \frac{1}{2} Li^2 = \frac{1}{2} \left(0.0200 \frac{\text{V} \cdot \text{s}}{\text{A}} \right) (19.5 \text{ A})^2 = \boxed{3.80 \text{ J}}$$

33.15

$$I_{\max} = \sqrt{2} I_{\text{rms}} = \frac{\sqrt{2} (\Delta V_{\text{rms}})}{X_C} = \sqrt{2} (\Delta V_{\text{rms}}) 2\pi f C$$

$$(a) \quad I_{\max} = \sqrt{2} (120 \text{ V}) 2\pi(60.0 / \text{s})(2.20 \times 10^{-6} \text{ C} / \text{V}) = \boxed{141 \text{ mA}}$$

$$(b) \quad I_{\max} = \sqrt{2} (240 \text{ V}) 2\pi(50.0 / \text{s})(2.20 \times 10^{-6} \text{ F}) = \boxed{235 \text{ mA}}$$

33.47

$$(a) \quad R = (4.50 \times 10^{-4} \, \Omega / \text{m})(6.44 \times 10^5 \text{ m}) = 290 \, \Omega$$

$$\text{and} \quad I_{\text{rms}} = \frac{\mathcal{P}}{\Delta V_{\text{rms}}} = \frac{5.00 \times 10^6 \text{ W}}{5.00 \times 10^5 \text{ V}} = 10.0 \text{ A}$$

$$\mathcal{P}_{\text{loss}} = I_{\text{rms}}^2 R = (10.0 \text{ A})^2 (290 \, \Omega) = \boxed{29.0 \text{ kW}}$$


$$(b) \quad \frac{\mathcal{P}_{\text{loss}}}{\mathcal{P}} = \frac{2.90 \times 10^4}{5.00 \times 10^6} = \boxed{5.80 \times 10^{-3}}$$

(c) It is impossible to transmit so much power at such low voltage. Maximum power transfer occurs when load resistance equals the line resistance of 290 Ω , and is

$$\frac{(4.50 \times 10^3 \text{ V})^2}{2 \cdot 2(290 \, \Omega)} = 17.5 \text{ kW}, \quad \text{far below the required } 5000 \text{ kW}$$

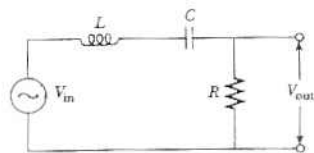*33.51

$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$



(a) At 200 Hz:
$$\frac{1}{4} = \frac{(8.00 \Omega)^2}{(8.00 \Omega)^2 + \left[400\pi L - \frac{1}{400\pi C}\right]^2}$$

At 4000 Hz:
$$(8.00 \Omega)^2 + \left[8000\pi L - \frac{1}{8000\pi C}\right]^2 = 4(8.00 \Omega)^2$$

At the low frequency, $X_L - X_C < 0$. This reduces to
$$400\pi L - \frac{1}{400\pi C} = -13.9 \Omega \quad [1]$$


For the high frequency half-voltage point,
$$8000\pi L - \frac{1}{8000\pi C} = +13.9 \Omega \quad [2]$$

Solving Equations (1) and (2) simultaneously gives
$$C = \boxed{54.6 \mu\text{F}} \quad \text{and} \quad L = \boxed{580 \mu\text{H}}$$

(b) When $X_L = X_C$,
$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \left(\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}}\right)_{\text{max}} = \boxed{1.00}$$

(c) $X_L = X_C$ requires
$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(5.80 \times 10^{-4} \text{ H})(5.46 \times 10^{-5} \text{ F})}} = \boxed{894 \text{ Hz}}$$

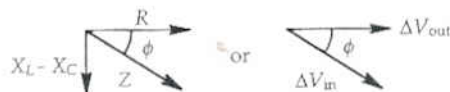(d) At 200 Hz, $\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{R}{Z} = \frac{1}{2}$ and $X_C > X_L$,



so the phasor diagram is as shown:

$$\phi = -\cos^{-1}\left(\frac{R}{Z}\right) = -\cos^{-1}\left(\frac{1}{2}\right)$$
 so
$$\Delta V_{\text{out}} \text{ leads } \Delta V_{\text{in}} \text{ by } 60.0^\circ$$

At f_0 , $X_L = X_C$ so
$$\Delta V_{\text{out}} \text{ and } \Delta V_{\text{in}} \text{ have a phase difference of } 0^\circ$$

At 4000 Hz, $\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{R}{Z} = \frac{1}{2}$ and $X_L - X_C > 0$

Thus,
$$\phi = \cos^{-1}\left(\frac{1}{2}\right) = 60.0^\circ$$



or
$$\Delta V_{\text{out}} \text{ lags } \Delta V_{\text{in}} \text{ by } 60.0^\circ$$

(e) At 200 Hz and at 4 kHz,
$$\mathcal{P} = \frac{(\Delta V_{\text{out,rms}})^2}{R} = \frac{\left(\frac{1}{2}\Delta V_{\text{in,rms}}\right)^2}{R} = \frac{\frac{1}{2}\left(\frac{1}{2}\Delta V_{\text{in,max}}\right)^2}{R} = \frac{(10.0 \text{ V})^2}{8(8.00 \Omega)} = \boxed{1.56 \text{ W}}$$

At f_0 ,
$$\mathcal{P} = \frac{(\Delta V_{\text{out,rms}})^2}{R} = \frac{(\Delta V_{\text{in,rms}})^2}{R} = \frac{\frac{1}{2}(\Delta V_{\text{in,max}})^2}{R} = \frac{(10.0 \text{ V})^2}{2(8.00 \Omega)} = \boxed{6.25 \text{ W}}$$

(f) We take:
$$Q = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R} = \frac{2\pi(894 \text{ Hz})(5.80 \times 10^{-4} \text{ H})}{8.00 \Omega} = \boxed{0.408}$$