

# MAE 106 Lab 3 Quiz and Midterm Exam Winter 2005

*Lab 3 Quiz = 100 pts*

University of California, Irvine  
Department of Mechanical and Aerospace Engineering

## Part 1: Lab 3 Quiz

In Lab 3, you built a motor velocity controller, using a proportional feedback control.

15 1. Write the velocity control law that you used for the motor in the box, where:

$u$  = the control input into the motor

$K$  = feedback gain

$\omega_{\text{actual}}$  = actual motor speed

$\omega_d$  = desired motor speed

$$u = -K(\omega_{\text{actual}} - \omega_d)$$

10 2. For the Lab 3 motor amplifier, the motor torque was proportional to the input.


$u = K(\omega_d - \omega_{\text{actual}})$   $\omega = K(\omega_{\text{actual}} - \omega_d)$   
 → ↓  
 OK ALSO

24 3. Below is the control circuit that you used to implement P-type velocity control. Briefly explain the purpose of each op-amp.

Op Amp 1: *Multiples  $\omega_d$  by -1 (inverts  $\omega_d$ )*

Op Amp 2: *Implements control law  $u = -K(\omega_{\text{actual}} - \omega_d)$*

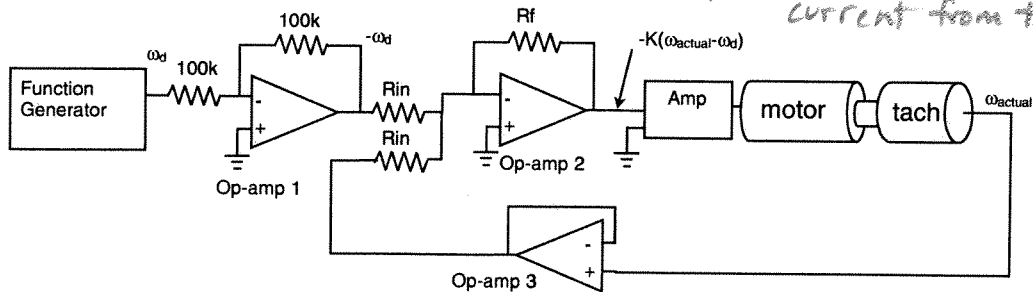Op Amp 3: *Buffers tachometer so that rest of circuit does not draw current from tach.*



24 4. Fill out the below chart based on your experience in lab:

Increasing $R_f$ will (circle one)		
Increase or decrease	$f_{3db}$	Cutoff frequency
Increase or decrease	$\tau = 1/\omega_{3db}$	Time constant
Increase or decrease	$e_{ss}$	Steady state error

15 5. The controlled motor behaved like what kind of filter? *Low pass filter*

12 6. At the cutoff frequency of the motor, the output amplitude was .707 of the input amplitude and the output waveform lagged the input by 45 degrees.

## Part 2: Midterm

### Problem 1 (10 Pts Extra Credit)

An oscilloscope is used to measure this:

2 Answer b a) resistance b) voltage c) current d) power

The time constant of a first-order system tells when the output has gotten how far along the way to its final value?

2 Answer c a) 37% b) 10% c) 63% d) 90%

If you put a sine wave into a linear system, you get the following out

2 Answer d a) square wave  
b) sine wave at different frequency  
c) triangle wave  
d) sine wave at same frequency, scaled and shifted

A filter scales a sinusoidal input. The amount of scaling is determined by:


2 Answer a a) the magnitude of the transfer function, evaluated at  $s=j\omega$   
b) the magnitude of the transfer function, evaluated at  $s = \omega$   
c) the phase of the transfer function, evaluated at  $s=j\omega$

A low pass filter attenuates

2 Answer b a) low frequencies  
b) high frequencies  
c) a band of frequencies

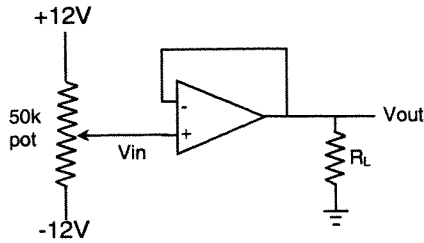**Problem 2 (25 pts)**

How close is  $V_{out}$  to  $V_{in}$  for the following voltage follower circuit, if the op-amp gain is 1,000?  
 (Hint, use the fact that  $V_o = K(V_+ - V_-)$  for the op amp)



$$V_{out} = K(V_+ - V_-)$$

$$= K(V_{in} - V_{out})$$


$$V_{out}(1+K) = K V_{in}$$

$$V_{out} = \frac{K}{1+K} V_{in} = \frac{1000}{1001} V_{in}$$

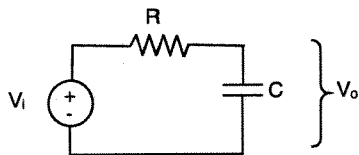**Problem 3 (25 pts)**

How does the following circuit filter a low frequency input? Specifically, find what the resulting scaling and phase-shift would be for an input sinusoid with a frequency of  $\frac{1}{2\pi} = 0.16$  Hz.

Assume  $R = 1$  kilohm and  $C = 1$  milliFarad.



Transfer function using impedances:

$$V_o = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i = \frac{1}{1 + RCs} V_i$$

$$H(s) = \frac{1}{1 + RCs}$$

5 pts  $\rightarrow H(j\omega) = \frac{1}{1 + RCj\omega}$

Scaling =  $|H(j\omega)| = \frac{1}{\sqrt{1 + (RC\omega)^2}}$

$= \frac{1}{\sqrt{2}} = 0.707$

$\omega = 2\pi f$

$= (2\pi) \left(\frac{1}{2\pi}\right) = 1 \text{ rad/sec}$

$RC = 1 \text{ sec}$

10 pts


phase =  $0 - \tan^{-1} \frac{RC\omega}{1} = -\tan^{-1} RC\omega = -\tan^{-1} 1$

10 pts  $\rightarrow$

$= 45^\circ \text{ or } \frac{\pi}{4}$

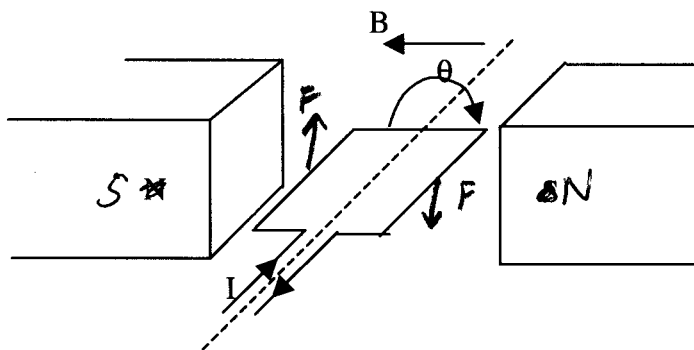Problem 4: 25 pts


- 5 a. Shown below is a diagram of a DC brushed motor. Assume that the commutation stops working, such that current flows only in the direction shown. At what angle  $\theta$  will the armature come to rest? Assume the armature is initially at  $\theta = 0^\circ$  as shown when the commutation fails, and that positive  $\theta$  is defined clockwise looking into the page, as shown.



$$F = i \vec{\ell} \times \vec{B}$$

$$\theta = 90^\circ$$

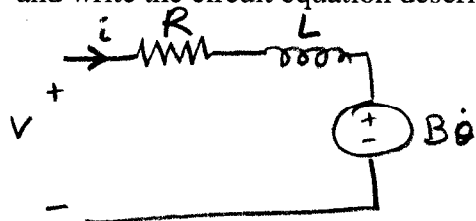- 5 b. For the rest of this problem, assume the commutation is working. Draw the circuit model, and write the circuit equation describing the motor:



$$V = Ri + L \frac{di}{dt} + B\dot{\theta}$$

- 15 b. Solve this differential equation for the current through the motor as a function of time when:
- the shaft of the motor is held fixed
  - a constant voltage  $v$  is applied across the motor at time = 0
  - the initial current  $i(t=0)$  through the inductor is zero

Shaft fixed  $\Rightarrow \dot{\theta} = 0$

$$L \frac{di}{dt} + Ri = V$$

Soln to homog. eqn:

$$\frac{di}{dt} = -\frac{R}{L} i \Rightarrow i = Ae^{-t/\tau} \quad \tau = \frac{L}{R}$$

Part. Soln:


$$i = \frac{V}{R}$$

Total Soln:  $i = Ae^{-t/\tau} + \frac{V}{R}$  but  $i(0) = 0$

$$\Rightarrow \boxed{i = \frac{V}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R}}$$


**Problem 5: 25 pts**

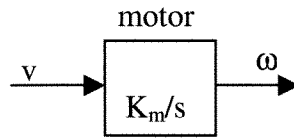- 1) You want to control the speed of a motor. You are using a current amplifier with the motor, so the speed is related to the input voltage to the current amplifier by the following transfer function:




where  $v$  is the voltage input to the motor and  $\omega$  is the angular velocity of the shaft and  $K_m$  is a constant.

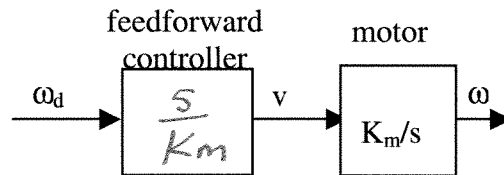- 10 pts a) Shown below is a block diagram of an open-loop (i.e. feedforward) controller for the motor, where  $\omega_d$  is the desired output of the motor. What transfer function should the controller box have to make the output equal the desired output? Write this function controller box.



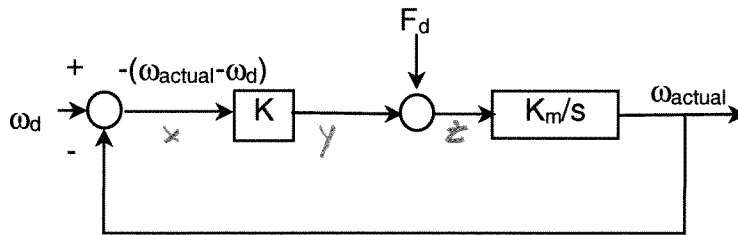- 15 pts b) One of the major benefits of feedback is its ability to cancel the effects of unmodeled "disturbances". Assume you build a feedback controller, but there is a disturbance force  $F_d$  affecting the motor:



Derive an expression that relates  $\omega_{actual}$  to  $\omega_d$  and  $F_d$ , then prove that the disturbance is cancelled if  $K$  is large enough.

10 pts

$$x = \omega_d - \omega_{actual}$$

$$y = Kx = K(\omega_d - \omega_{actual})$$

$$z = y + F_d$$

$$\omega_{actual} = \frac{K_m}{s} z = \frac{K_m}{s} (K(\omega_d - \omega_{actual}) + F_d)$$

$$s\omega_{actual} = K_m K \omega_d - K_m K \omega_{actual} + K_m F_d$$

$$\omega_{actual} (s + K_m K) = \frac{K_m K}{s} \omega_d + \frac{K_m}{s} F_d$$

$$\omega_{actual} = \frac{K_m K}{s + K_m K} \omega_d + \frac{K_m}{s + K_m K} F_d$$

5 pts

as  $K \rightarrow \infty$   
 $\omega_{actual} \rightarrow \omega_d$