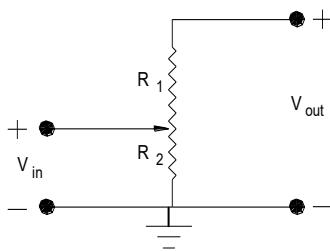


# MAE 106 Midterm Exam Winter 2002


University of California, Irvine  
Department of Mechanical and Aerospace Engineering

## Problem 1: Circuits (25 pts)

- a) Shown below is a 10Kohm potentiometer wired incorrectly. Assume  $V_{in}$  is 10 V and is provided by a 100 Watt power supply. Assume the potentiometer is rated at 1 Watt. Assume the shaft can rotate 180 degrees, and define 0 degrees rotation as the shaft angle when the resistance between the wiper and the ground is 10Kohm. At what shaft angle do you expect to smell smoke?



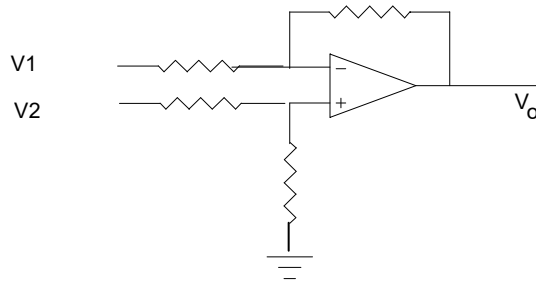- b) What does the following circuit do? (give proof) Assume the four resistors have equal values.




- c) Why are op amps such as the ones used in lab unsatisfactory for powering most motors?

- d) Assume that you have a low-power control signal from a computer, and that you would like to make a motor spin when the control signal is +5 v, and to stop spinning when the control signal is 0 V. Design a circuit using a MOSFET to achieve this control.




**Problem 3: Control Theory (25 pts)**

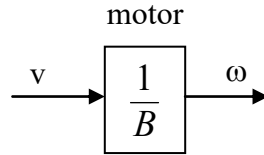- 1) Consider the problem of controlling the velocity of a motor. A simple model of the motor is given by the following block diagram:



where  $v$  is the voltage input to the motor and  $\omega$  is the angular velocity of the shaft.

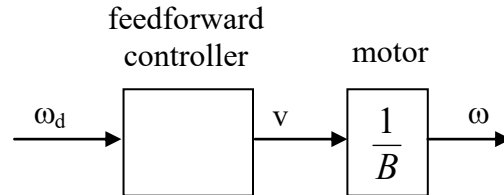
- a) Shown below is a block diagram of an open-loop (i.e. feedforward) controller for the motor, where  $\omega_d$  is the desired output of the motor. What gain value should the controller box have to make the output equal the desired output? Write the gain in the controller box.



- b) Name two disadvantages and two advantages of an open-loop controller like this one.
- c) Draw a block diagram of a feedback controller for the motor, label all arrows, including the error signal.
- d) Prove that your feedback controller cancels an additive disturbance  $V_d$  to the voltage input to the motor, given a high enough feedback gain.

**Problem 4: Signal Processing, Differential Equations, and Frequency Analysis (25 pts)**

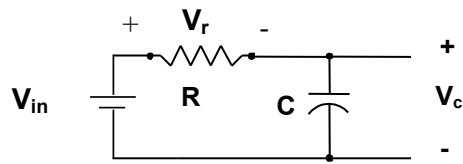a) Describe a practical situation in which the following circuit would be useful:



b) Assume  $V_{in}$  is a step input at time zero and  $V_c(0) = 0$ . Find  $V_c(t)$ .

c) Find the transfer function for the above circuit.

d) Find the frequency response of the above circuit. Be sure to provide equations for how the circuit scales and phase shifts a sinusoidal input.

e) Assume  $R = 100$  ohm,  $C = .01$  F. How much more attenuated will a 1000 Hz sinusoidal input signal be than a 100 Hz input signal? (Provide proof).